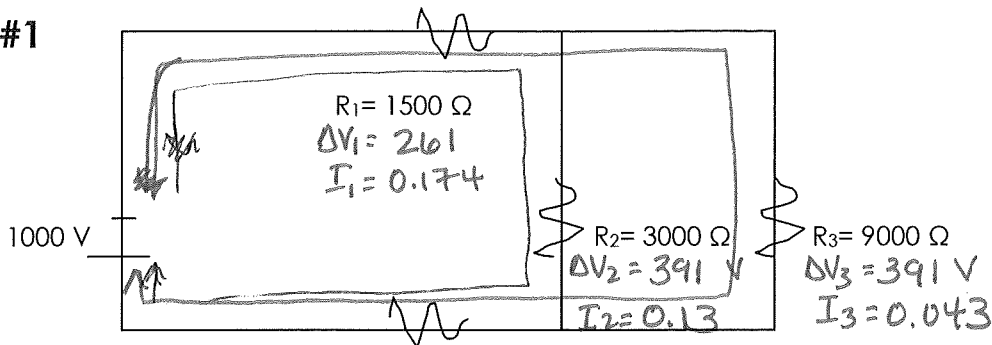


# Complex Circuit Practice Worksheet

## Circuit #1



$R_4 = 2000 \Omega$   
 $\Delta V_4 = 348 \text{ V}$   
 $I_4 = 0.174$

1. Find the **total resistance**. (Do parallel resistors first-get an answer, then add the series ones)  
 (5750  $\Omega$ )

$$\frac{1}{R_{eq}} = \frac{1}{3000} + \frac{1}{9000} \quad R_{eq} = 2250 + 1500 + 2000 = \boxed{5750 \Omega}$$

2. Find the **total current**. (Round to 3 decimals!) (0.174 A)

$$\Delta V = IR \quad 1000 = I(5750) \quad \boxed{I = 0.174 \text{ A}}$$

3. Find the voltage drop for any resistors in series. (There should be 2 series resistors)  
 ( $\Delta V_1 = 261 \text{ V}$ ,  $\Delta V_4 = 348 \text{ V}$ )

$$R_1: \Delta V_1 = (.174)(1500) = 261 \text{ V} \quad R_4: \Delta V_4 = (.174)(2000) = 348 \text{ V}$$

4. Find the voltage lost through resistor 2. (Remember- each circuit path adds up to the total voltage of the battery) ( $\Delta V_1 + \Delta V_2 + \Delta V_4 = 1000 \text{ V}$ )

$$\Delta V_1 + \Delta V_2 + \Delta V_4 = 1000 \text{ V} \quad \Delta V_2 = 391 \text{ V}$$

$$261 + \Delta V_2 + 348 = 1000$$

5. Find the voltage lost at R3.  
 ( $\Delta V_1 + \Delta V_3 + \Delta V_4 = 1000 \text{ V}$ )

same 391 V

6. Solve for the currents through the rest of the resistors and put your answers in the box.

$$R_2: \Delta V_2 = I_2 R_2$$

$$391 = I_2(3000)$$

$$I_2 = .13$$

$$R_3: \Delta V_3 = I_3 R_3$$

$$391 = I_3(9000)$$

$$I_3 = 0.043$$


7. What is  $I_2 + I_3$ ? Does it equal the total current? It SHOULD!

$$\begin{array}{r} .13 \\ + .043 \\ \hline .173 \checkmark \end{array}$$

$I_1 = \underline{.174 \text{ A}}$	(0.174 A)
$I_2 = \underline{0.13 \text{ A}}$	(0.130 A)
$I_3 = \underline{0.043 \text{ A}}$	(0.043 A)
$I_4 = \underline{.174 \text{ A}}$	(0.174 A)
$\Delta V_1 = \underline{261 \text{ V}}$	(261 V)
$\Delta V_2 = \underline{391 \text{ V}}$	(391 V)
$\Delta V_3 = \underline{391 \text{ V}}$	(391 V)
$\Delta V_4 = \underline{348 \text{ V}}$	(348 V)

# Complex Circuit Practice Worksheet

## Circuit #2

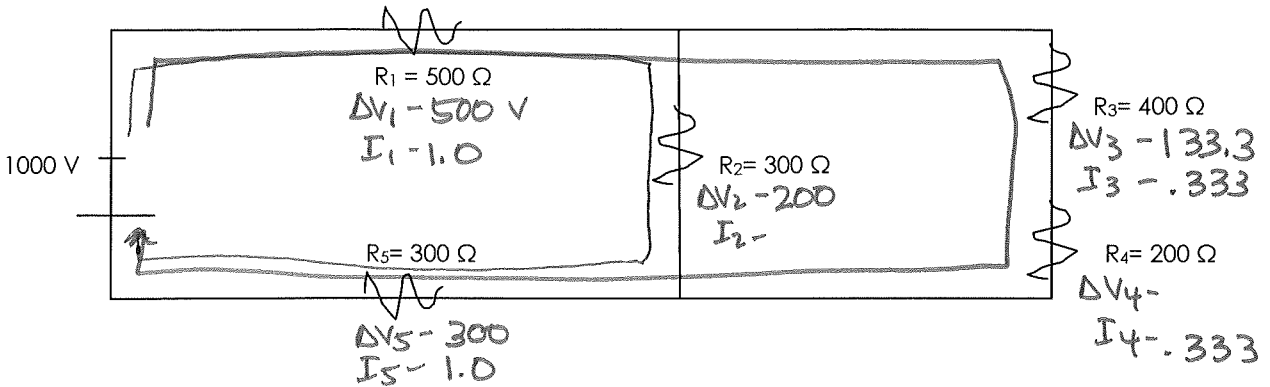

1. Find the **total resistance**. ( $R_3$  and  $R_4$  are in series with each other but in parallel with  $R_2$ , so do  $\frac{1}{300} + \frac{1}{(400+200)}$ , get an answer and then add the two resistors that are in series.)

$$\frac{1}{R_{eq}} = \frac{1}{300} + \frac{1}{600} = 200\Omega + 500 + 800 = \boxed{1000\Omega}$$

2. Find the total current. (Use the total voltage and total resistance) (1.0 A)

$$\Delta V = IR$$

$$1000 = I(1000)$$

$$\boxed{I = 1.0 \text{ A}}$$

8. Find the voltage drop for any resistors that are in series.

( $\Delta V_1 = 500 \text{ V}$ ,  $\Delta V_5 = 300 \text{ V}$ )

$$\Delta V_1 = (1)(500) = 500 \text{ V}$$

$$\Delta V_5 = (1)(300) = 300 \text{ V}$$

9. Find the voltage lost at  $R_2$  and then the current through it.

( $\Delta V_1 + \Delta V_2 + \Delta V_5 = 1000 \text{ V}$ )

$$1000 = 500 + \Delta V_2 + 300$$

$$\boxed{\Delta V_2 = 200 \text{ V}}$$

$$200 = I_2(300)$$

$$I_2 = .667$$

10. What is the voltage left to be lost through  $R_3$  and  $R_4$ ?

$$200 \text{ V}$$

11. Use this voltage and their combined resistance to find the current through  $R_3$  and  $R_4$ . (It's the same).

$$\Delta V = IR$$

$$200 = I(400+200)$$

$$\boxed{I = .333 \text{ A}}$$

12. Find the voltage of  $R_3$  using the current you just found.

$$\Delta V_3 = IR$$

$$\Delta V_3 = (.333)(400) = \boxed{133.3 \text{ V}}$$

13. Find the voltage of  $R_4$ .

$$\Delta V_4 = (.333)(200) = \boxed{66.6 \text{ V}}$$

14. What is  $\Delta V_1 + \Delta V_2 + \Delta V_5$ ? Does it equal  $\Delta V_1 + \Delta V_3 + \Delta V_4 + \Delta V_5$ ? Explain why it should!

$$1000$$

$$500 + 200 + 300 = 1000$$

$$500 + 133.3 + 66.6 + 300 = 999.9 \checkmark$$

$I_1 =$	<u>1.0 A</u>	(1.0 A)
$I_2 =$	<u>.667 A</u>	(0.667 A)
$I_3 =$	<u>.333 A</u>	(0.333 A)
$I_4 =$	<u>.333 A</u>	(0.333 A)
$I_5 =$	<u>1.0 A</u>	(1.0 A)
$\Delta V_1 =$	<u>500 V</u>	(500 V)
$\Delta V_2 =$	<u>200 V</u>	(200 V)
$\Delta V_3 =$	<u>133.3 V</u>	(133.2 V)
$\Delta V_4 =$	<u>66.6 V</u>	(66.6 V)
$\Delta V_5 =$	<u>300 V</u>	(300 V)