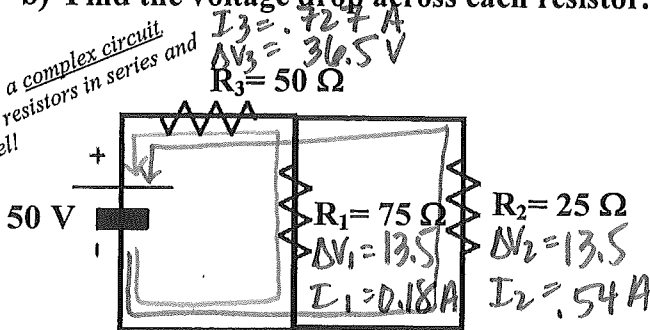


- Problem 4** a) Find the current in each resistor.
 b) Find the voltage drop across each resistor.

This is known as a complex circuit.
 There are some resistors in series and some in parallel!



Step #1- Find the total resistance.

(For a complex circuit, use $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ for those resistors

that are in parallel, solve for that R_T , then add those that are in series to that total.)

Step #2- Use Ohm's Law to find the total current.

Step #3- Answer the questions.

$$R_{eq} = 68.75 \Omega$$

$$\text{Current} = 0.727 A$$

Parallel + series

① $\frac{1}{R_{eq}} = \frac{1}{75} + \frac{1}{25}$ $R_{eq} = 18.75 + 50 = 68.75 \Omega$

④ 2 closed loops

② Total current
 $\Delta V = I R$
 $50 = I(68.75)$
 $I = 0.727 A$

① ~~50V~~ $50V = \Delta V_1 + \Delta V_3$
 $50 = \Delta V_1 + 36.5V$
 $\Delta V_1 = 13.5V$

③ All current goes through R_3
 so start there

② $50V = \Delta V_2 + \Delta V_3$
 $50 = \Delta V_2 + 36.5$
 $\Delta V_2 = 13.5V$

should be same

$\Delta V_3 = I_3 R_3$
 $\Delta V_3 = (0.727)(50) = 36.5V$

⑤ Now find currents

$\Delta V_1 = I_1 R_1$	$\Delta V_2 = I_2 R_2$
$13.5 = I_1(75)$	$13.5 = I_2(25)$
$I_1 = 0.18 A$	$I_2 = 0.54 A$

⑥ check answers
 Total current $.18 + .54 = .72 \checkmark$
 Total ΔV $36.5 + 13.5 = 50 \checkmark$