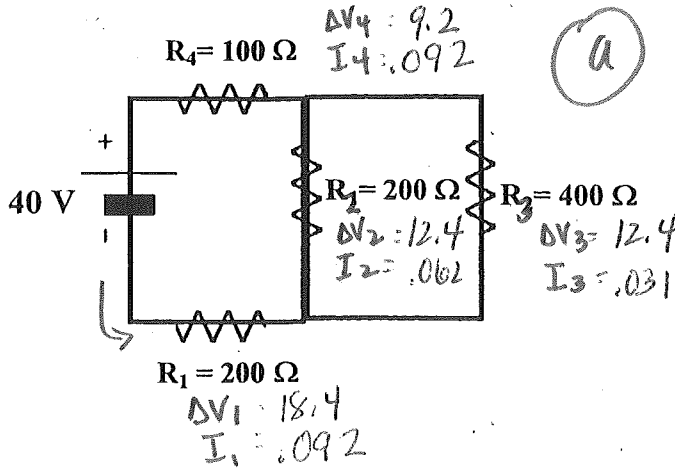


- Problem 4**
- Find the voltage drop across each resistor.
  - Find the current through each resistor.



(a)  $\Delta V_1 = (.092)(200 \Omega) = 18.4 \text{ V}$

$\Delta V_4 = (.092)(100) = 9.2 \text{ V}$

$40 = \Delta V_1 + \Delta V_2 + \Delta V_4$   
 $18.4 + \Delta V_2 + 9.2$

$\Delta V_2 = 12.4 \text{ V}$

$\Delta V_3 = 12.4 \text{ V}$

① Find  $R_{eq}$

$\frac{1}{R_{eq}} = \frac{1}{200} + \frac{1}{400}$   $R_{eq} = 133.3 \Omega$

$133.3 \Omega + 200 \Omega + 100 \Omega = 433.3 \Omega$

(b) Find  $I_2 + I_3$

$\Delta V_2 = I_2 R_2$

$12.4 = I_2 (200)$

$I_2 = .062 \text{ A}$

$\Delta V_3 = I_3 R_3$

$12.4 = I_3 (400)$

$I_3 = .031 \text{ A}$

② Total current

$\Delta V = I R$

$40 \text{ V} = I (433.3 \Omega)$

$I = .092 \text{ A}$

total current

$.092 = .062 + .031$  ✓

✓  $\Delta V \ 40 =$