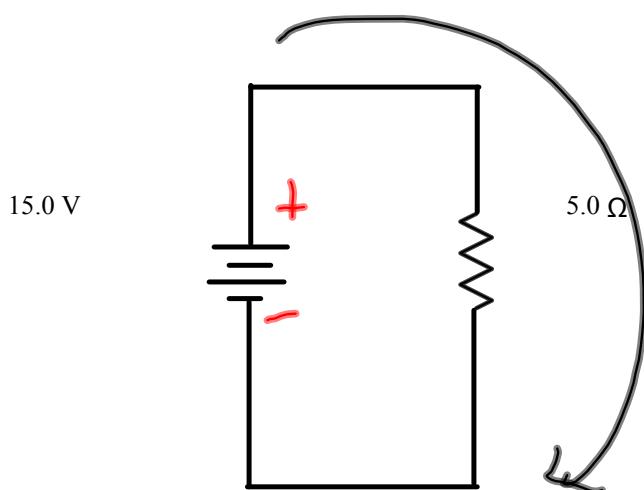


Electric Circuits:

Ohms Law:

$$V=IR$$

$$I = \frac{V}{R} = 3A$$



$V = \text{Voltage} = DOP = \xi mf$

Measured in Volts

$R = \text{Resistance}$

Measured in Ohms



$I = \text{Current}$

Measured in Amperes or amps

Series Circuits

Current is constant


Resistance is additive

$$R_T = R_1 + R_2 + R_3$$

$$V_T = V_1 + V_2 + V_3$$


$$R_1 = R_2 = R_3 = 1\Omega \quad I_T = I_1 = I_2 = I_3$$

$$R_T = 3\Omega$$

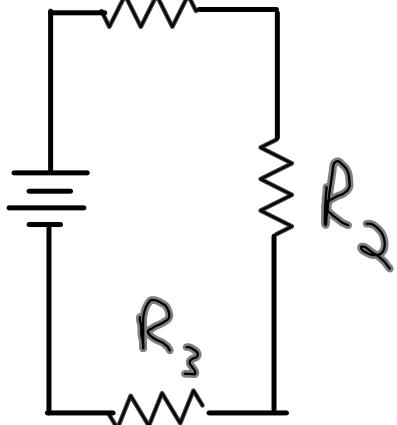

Parallel Circuits
Voltage is constant
Current is additive


$$R_T = \frac{1}{3} \Omega$$

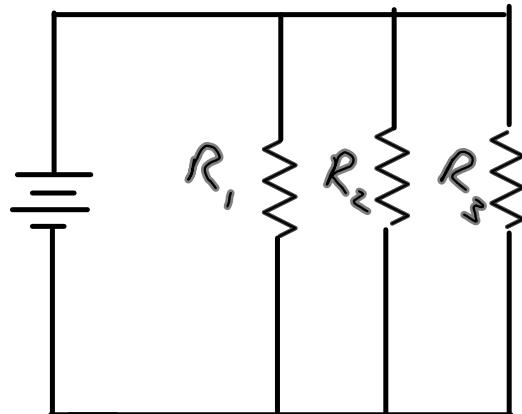


$$V_T = V_1 = V_2 = V_3$$

$$I_T = I_1 + I_2 + I_3$$
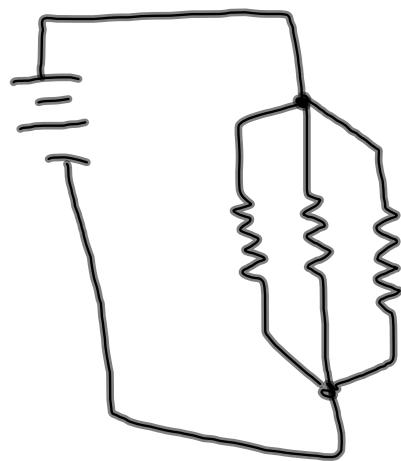
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



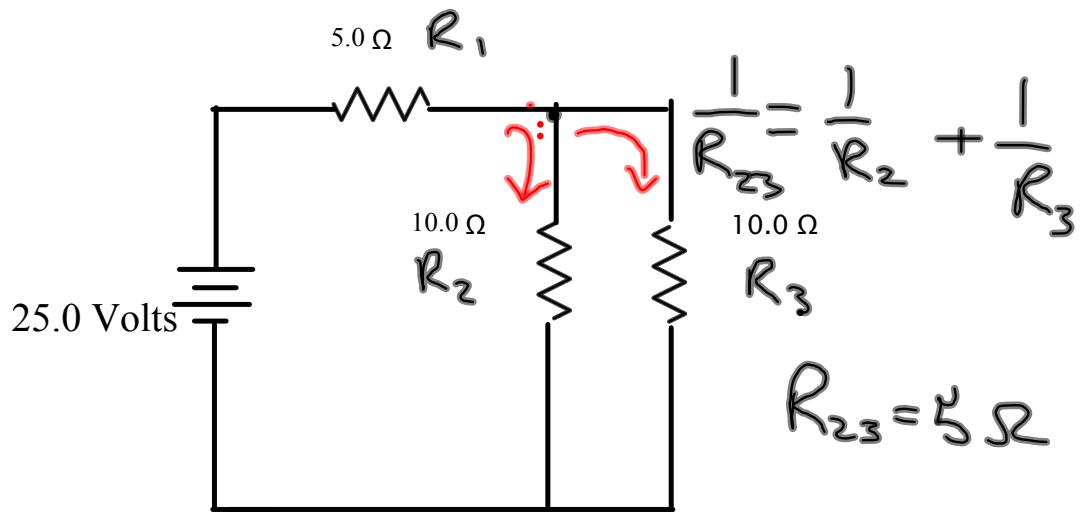

$$V_t = 25 \text{ V}$$

$$V_1 = I \cdot R_1 = 12.5 \text{ V}$$

$$V_2 = 12.5 \text{ V}$$

$$V_3 = 12.5 \text{ V}$$

$$R_t = 10 \Omega$$

$$R_1 = 5 \Omega$$

$$R_2 = 10 \Omega$$

$$R_3 = 10 \Omega$$

$$I_t = \frac{V_t}{R_T} = 2.5 \text{ A}$$

$$I_1 = 2.5 \text{ A}$$

$$I_2 = 1.25 \text{ A}$$

$$I_3 = 1.25 \text{ A}$$

