

# How Potato Batteries Work

## The Powerful Potato

Potatoes are great mashed, roasted, baked or in **clocks**. That's right, potatoes are nature's tastiest [battery](#). Check out the 411 on the science behind this **powerfully delicious** snack.



## How to Make a Potato Battery

Making a clock run on **potato power** is easier than you might think. This project is easy, [bizarre](#) and makes a sweet [science fair project](#) or chemistry experiment. Who knew potatoes could be so **empowering**?

### What You Need:

- Two Potatoes
- Two short pieces of **heavy copper** wire
- Two common galvanized nails
- Three [alligator](#) clip/wire units (alligator clips connected to each other with wire)
- One simple low-voltage **LED clock** that functions from a 1- to 2-volt button-type battery (Radio Shack)

### Steps:

1. Remove the **battery** from the battery compartment of the clock.
2. Make a note of which way around the [positive](#) (+) and a negative (-) points of the battery went.
3. Number the potatoes as one and two.
4. Insert **one nail** in each potato.
5. Insert one short piece of the copper wire into each potato as **far away** from the nail as possible.
6. Use one [alligator](#) clip to [connect](#) the copper wire in potato number one to the positive (+) terminal in the clock's battery compartment.
7. Use one alligator clip to connect the nail in **potato number two** to the negative (-) terminal in the clock's battery compartment.
8. Use the third alligator clip to **connect the nail** in potato one to the copper wire in potato two and [set the clock!](#)



## How the Potato Clock works

A potato battery is an **electrochemical battery**, otherwise known as an electrochemical cell. An electrochemical cell is a cell in which [chemical](#) energy is converted to [electric energy](#) by a spontaneous electron transfer. In the case of the potato, the zinc in the nail reacts with the copper wire. The potato acts as a sort of buffer between the **zinc ions** and the **copper ions**. The zinc and copper ions would still react if they touched within the potato but they would only **generate heat**. Since the potato keeps them apart, the electron transfer has to take place over the copper wires of the circuit, which channels the [energy](#) into the clock. Presto! You have potato power.