

Content Practice A

LESSON 3

Describing Circuits

Directions: On the line before each statement, write T if the statement is true or F if the statement is false. If the statement is false, change the underlined words(s) to make it true. Write your changes on the lines provided.

- T 1. Electric circuits can have one or multiple paths. _____
- T 2. In an open path, electric current stops flowing. _____
- F 3. The basic parts of an electric circuit include the source of energy, electric devices, and parallel circuits. _____
- T 4. In a series circuit, electric current flows along a single path.

- T 5. One type of energy transformation by an electric device is electric energy transformed to thermal energy. _____
- F 6. Adding a fan and an electric light to a parallel circuit decreases the electric current flowing in the circuit. _____
- F 7. A series circuit can be broken or open. _____
- T 8. A parallel circuit can have two or more branches. _____
- T 9. Wall switches in a home are used to open or close electric circuits.

- F 10. The turning of a fan is an example of the transformation of electric energy to light energy. _____
- T 11. A battery can serve as a source of chemical energy. _____
- T 12. Never touch a downed electric wire. _____